

Ohm's Law $V=IR$, where V=voltage in volts, I=current in amperes, and R=resistance in ohms

DC Circuits

Resistors in Series: The same current goes through all of the resistors.

The equivalent series resistor to 3 resistors in series has the resistance

$$R_{\text{series}} = R_1 + R_2 + R_3$$

Resistors in Parallel have the same voltage.

For 3 resistors in parallel, $V=V_1=V_2=V_3$

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_{\text{par}}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Kirchhoff's Laws

1. **Current Law** : from charge conservation at a node
 - a. $\sum I_{\text{in}} = 0$, i.e., the sum of all currents coming into a node =0.
 - b. $\sum I_{\text{in}} = \sum I_{\text{out}}$, i.e., the sum of all currents into node = the sum of all currents leaving
2. **Voltage Law**: from energy conservation around a closed loop
 - a. $\sum_{\text{around closed loop}} \Delta V = 0$.