

- Rules
1. Op-amp makes the 2 input voltages the same.
 2. Inputs draw no current.
 3. Use with feedback.

Inverting amplifier




$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Non-inverting amplifier


$$V_{in} = V_A$$

$$V_A = \frac{V_{out} R_1}{R_1 + R_2}$$

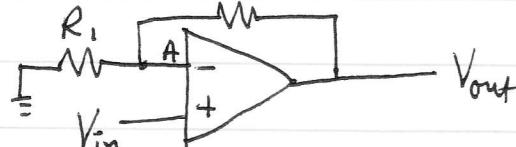


$$\text{Gain} = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

Follower

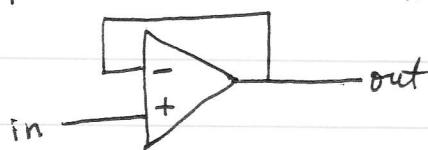


unity gain = buffer (isolating properties)
high input impedance, low output impedance

Differential amplifier

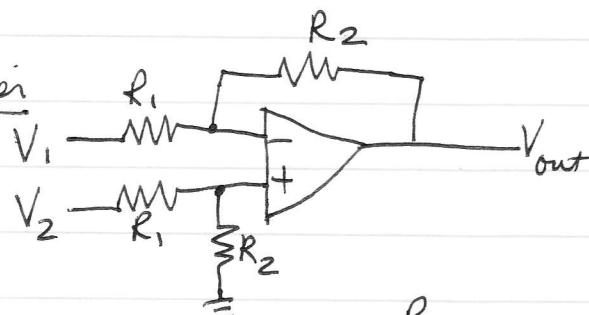


$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Summing amplifier

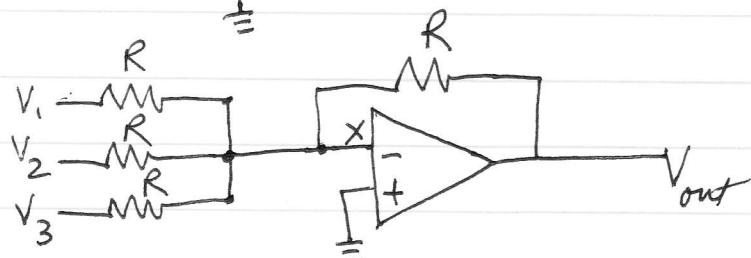


X is virtual ground.
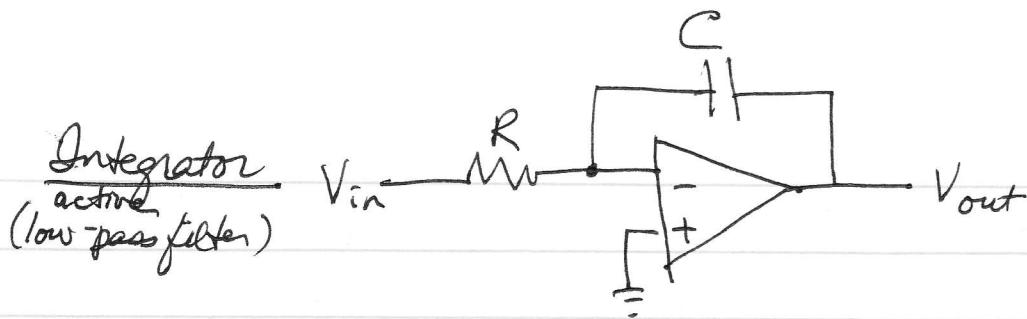
$$\text{Input current} = \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R} = \text{output current} = \frac{V_{out}}{R}, \quad V_{out} = -(V_1 + V_2 + V_3)$$



$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$
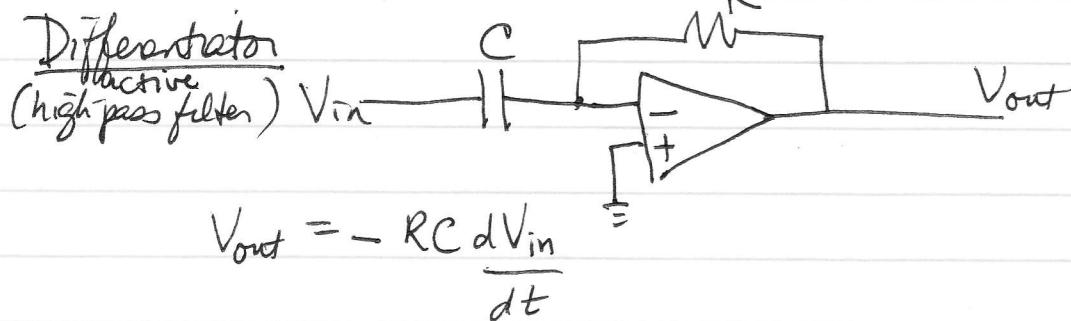
$$V_{out} = -\frac{1}{RC} \int V_{in} dt + \text{constant}$$



$$V_{out} = -RC \frac{dV_{in}}{dt}$$